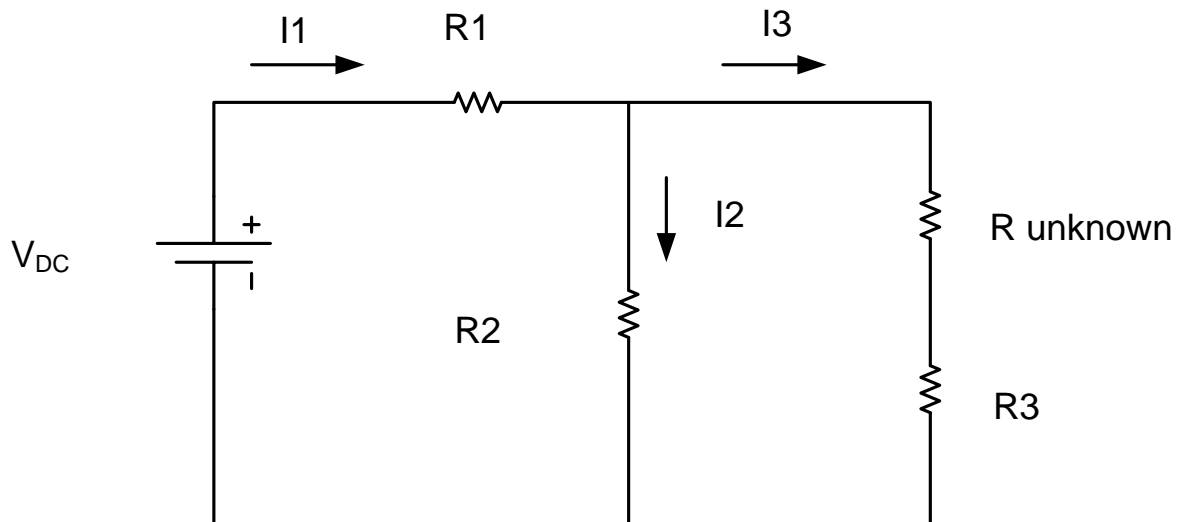


ECE2274
Practice Final Exam B

1. (25 points) Build the circuit below and calculate current by measuring voltage across a known resistor. Find the total current (I_1) and each of the branch circuit currents (I_2) and (I_3). Note: you may need more measurements than just current. Calculate the value of the unknown resistor (given for practice exam). Must show work and include units. Must include units.

$V_{DC} = 10V_{DC}$, $R_1 = 220\Omega$, $R_2 = 2.7K\Omega$, $R_3 = 1K\Omega$ let $R_{unknown} = 560$ for practice

I_1		I_2	
I_3		$R_{unknown}$	




ECE2274
Practice Final Exam B

2. Build the circuit below and measure V_{OUT} peak and the V_{RIPPLE} peak to peak with the oscilloscope. Include AC coupled scope capture of V_{RIPPLE} . Measure the actual value of the capacitor. Must include units.

$V_{in} = 10\sin(2\pi 1000t) + 0$, $C1 = 10\mu F$, $R_{load} = 1K\Omega$, $D1 = 1N4001$

Vin Frequency in Hz		V_{OUT} peak	
C measured		V_{RIPPLE}	

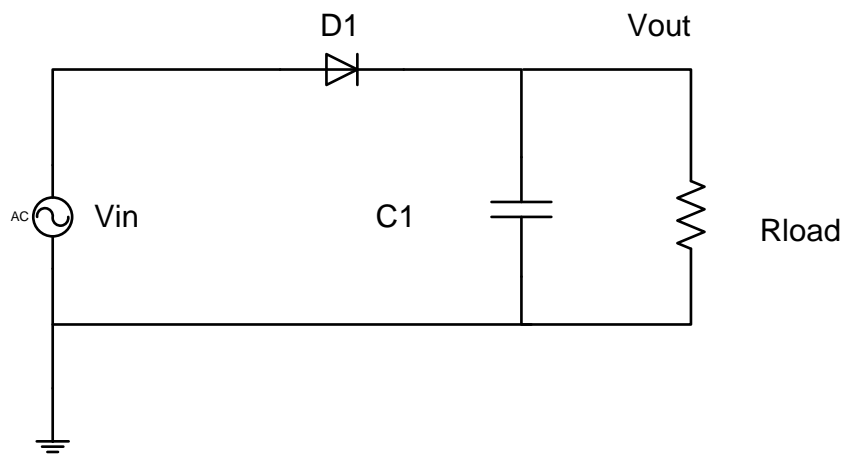


3. RC Circuit

1 build the RC circuit run AC sweep from 10 Hz to 300 kHz. $V_{in} = 1V_{pp}$

2. Cutoff break point from the Gain plot

Breakpoint Gain (dB) _____ Frequency _____ Filter Type _____

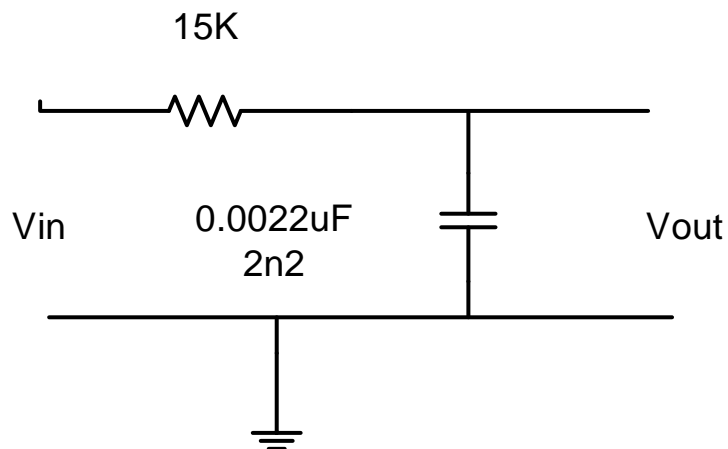

ECE2274
Practice Final Exam B

4 a. Build the circuit below you will need two supplies and using the DC sweep on the computer find the V_{TN} (threshold voltage) by sweeping the V_{GS} DC supply from 0Vdc to 5Vdc until you observe I_D of 0.1ma for the 2N7000 MOSFET. Must include units. $V_{DD} = 12V_{dc}$, $R_{load} = 1K\Omega$, $V_{GS} = 0V$ to 5V Include plot. Add a step to plot the I_d current in mA. Cannot use a current meter.

V_{TN}	
----------	--

4 b.(25 points) Also measure V_{DS} and I_{DS} using the meters only for the (off state) $V_{GS} = 0V_{DC}$ and the (on state) $V_{GS} = 5V_{dc}$. Must include units. Do not use current meter.

$V_{GS}(\text{off})$	0 V_{DC}	$V_{GS}(\text{on})$	5 V_{DC}
$V_{DS}(\text{off})$		$V_{DS}(\text{on})$	
$I_{DS}(\text{off})$		$I_{DS}(\text{on})$	

$V_{DD} = 12V_{dc}$, $R_{load} = 1.5K\Omega$, $V_{GS} = \text{variable}$

